

7. A toaster has a resistance of $60\ \Omega$ and is plugged into a power supply that needs $240\ \text{J}$ of energy to move $2\ \text{C}$ of charge, what is the current in the toaster?

$$\begin{array}{l}
 E = 240\ \text{J} \\
 Q = 2\ \text{C} \\
 V = x
 \end{array}
 \quad
 \begin{array}{l}
 V = \frac{240\ \text{J}}{2\ \text{C}} \\
 V = 120\ \text{V}
 \end{array}
 \quad
 \begin{array}{l}
 R = 60\ \Omega \\
 V = 120\ \text{V} \\
 I = x
 \end{array}
 \quad
 \begin{array}{l}
 60\ \Omega = \frac{120\ \text{V}}{x} \\
 \boxed{x = 2.67\ \text{A}} \\
 \text{The answer is 2 A}
 \end{array}$$

8. A circuit has a potential difference of $20\ \text{V}$ and draws a current $4.2\ \text{A}$ what is the resistance in the circuit?

$$\begin{array}{l}
 R = x \\
 V = 20\ \text{V} \\
 I = 4.2\ \text{A}
 \end{array}
 \quad
 \begin{array}{l}
 R = \frac{20\ \text{V}}{4.2\ \text{A}} \\
 \boxed{R = 4.76\ \Omega}
 \end{array}$$

9. A circuit has a potential difference of $60\ \text{V}$ and a current of $15\ \text{A}$, what is the resistance in the circuit?

$$\begin{array}{l}
 R = x \\
 V = 60\ \text{V} \\
 I = 15\ \text{A}
 \end{array}
 \quad
 \begin{array}{l}
 R = \frac{60\ \text{V}}{15\ \text{A}} = \boxed{4\ \Omega}
 \end{array}$$

10. A stove uses a power source of $240\ \text{V}$ and draws a current of $5.0\ \text{A}$ what is the resistance in the stove?

$$\begin{array}{l}
 R = x \\
 V = 240\ \text{V} \\
 I = 5.0\ \text{A}
 \end{array}
 \quad
 \begin{array}{l}
 R = \frac{240\ \text{V}}{5.0\ \text{A}} = \boxed{48\ \Omega}
 \end{array}$$

11. A dryer has a resistance of $800\ \Omega$ and draws a current of $0.30\ \text{A}$ what is the potential difference

$$\begin{array}{l}
 R = 800\ \Omega \\
 V = x \\
 I = 0.30\ \text{A}
 \end{array}
 \quad
 \begin{array}{l}
 800\ \Omega = \frac{x}{0.30\ \text{A}} \\
 \boxed{x = 240\ \text{V}}
 \end{array}$$

12. A radio has a power source of $6.0\ \text{V}$ and operates with a current of $0.40\ \text{A}$ what is the resistance in the circuit?

$$\begin{array}{l}
 R = x \\
 V = 6.0\ \text{V} \\
 I = 0.40\ \text{A}
 \end{array}
 \quad
 \begin{array}{l}
 R = \frac{6.0\ \text{V}}{0.40\ \text{A}} = \boxed{15\ \Omega}
 \end{array}$$