

Ohm's Law Worksheet

Answer the following questions by:

- Identify the variables you have
- Identify the variable you are missing
- Use the formula to find the missing variable

1. What is the voltage in a circuit that has a current of 2.4 A and a resistance of 4.0 Ω ?

$$R = 4.0 \Omega \quad 4.0 \Omega = \frac{x}{2.4 A} = \boxed{9.6 V}$$

$$V = x$$

$$I = 2.4 A$$

2. A circuit has a resistance of 12 Ω and draws a current of 6.0 A what is the potential difference in the circuit?

$$R = 12 \Omega \quad 12 \Omega = \frac{x}{6.0 A} = \boxed{72 V}$$

$$V = x$$

$$I = 6.0 A$$

3. A walkman uses a current of 2.0 A and has an internal resistance of 3.0 Ω , how many 1.5V batteries are required?

$$R = 3.0 \Omega \quad 3.0 \Omega = \frac{x}{2.0 A} \quad \frac{6.0 V}{1.5 V} = \boxed{4 \text{ batteries}}$$

$$V = x$$

$$I = 2.0 A$$

4. A TV set has 0.5 C pass through it in 5 s and has a resistance of 10 Ω , what is the potential difference?

$$I = x \quad I = \frac{0.5 C}{5 s} = 0.1 A \quad R = 10 \Omega \quad 10 \Omega = \frac{x}{0.1 A}$$

$$Q = 0.5 C$$

$$t = 5 s$$

$$V = x$$

$$I = 0.1 A \quad \boxed{x = 100 V}$$

The answer is 1V

5. A circuit has a potential difference of 20 V and has a resistance of 4.5 Ω , how much current will the circuit use?

$$R = 4.5 \Omega \quad 4.5 \Omega = \frac{20 V}{x}$$

$$V = 20 V$$

$$I = x \quad \boxed{x = 4.4 A}$$

6. A circuit has an internal resistance of 8.0 Ω and uses a potential difference of 12 V what is the current in the circuit?

$$R = 8.0 \Omega \quad 8.0 \Omega = \frac{12 V}{x}$$

$$V = 12 V$$

$$I = x \quad \boxed{x = 1.5 A}$$