

Ohm's Law Worksheet

Answer the following questions by:

- Identify the variables you have
- Identify the variable you are missing
- Use the formula to find the missing variable

1. What is the voltage in a circuit that has a current of 2.4 A and a resistance of 4.0 Ω ?

2. A circuit has a resistance of 12 Ω and draws a current of 6.0 A what is the potential difference in the circuit?

3. A walkman uses a current of 2.0 and has an internal resistance of 3.0 Ω , how many 1.5V batteries are required?

4. A TV set has 0.5 C pass through it in 5 s and has a resistance of 10 Ω , what is the potential difference?

5. A circuit has a potential difference of 20 V and has a resistance of 4.5 Ω , how much current will the circuit use?

6. A circuit has an internal resistance of 8.0 Ω and uses a potential difference of 12 V what is the current in the circuit?

7. A toaster has a resistance of $60\ \Omega$ and is plugged into a power supply that needs $240\ \text{J}$ of energy to move $2\ \text{C}$ of charge, what is the current in the toaster?

8. A circuit has a potential difference of $20\ \text{V}$ and draws a current $4.2\ \text{A}$ what is the resistance in the circuit?

9. A circuit has a potential difference of $60\ \text{V}$ and a current of $15\ \text{A}$, what is the resistance in the circuit?

10. A stove uses a power source of $240\ \text{V}$ and draws a current of $5.0\ \text{A}$ what is the resistance in the stove?

11. A dryer has a resistance of $800\ \Omega$ and draws a current of $0.30\ \text{A}$ what is the potential difference

12. A radio has a power source of $6.0\ \text{V}$ and operates with a current of $0.40\ \text{A}$ what is the resistance in the circuit?