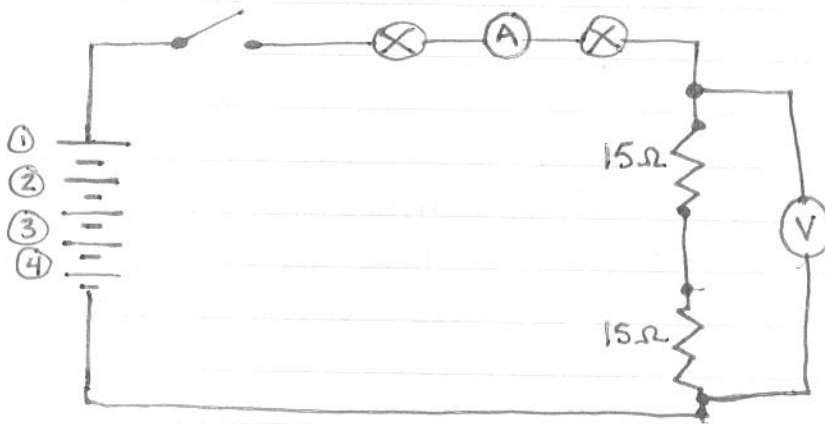


Circuit Diagrams

10)

$$V_T = 7.5\text{V}$$



Do not calculate TOTAL Resistance

11)

